

MODULE addsub
TITLE 'Adder/Subtractor with Flags'

" addsub DEVICE 'MACH4032'

" Description: This is the program for Homework #4. It implements a
" 4-bit Adder/Subtractor which includes flags summarizing the
" result (zero, carry/borrow, overflow, and sign). It also has
" outputs that output the comparison result (assuming a
" subtraction is being done).

" Revision History:

" 04/24/07 Glen George Initial Revision
" 04/25/07 Glen George Fixed logic so add and subtract both work and fit
" 04/25/07 Glen George Fixed reversal of SignedGT and SignedLT outputs
" (label on PCB is wrong)
" 10/24/07 Glen George Changed pinout and Subtract polarity to match new
" PCB
" 10/24/07 Glen George Changed file to match the new assignment
" 10/24/07 Glen George Updated comments
" 11/02/08 Glen George Updated comments
" 01/12/18 Glen George Changed pinout to match new PCB (v3.0)
" 01/04/21 Glen George Updated comments
" 02/03/23 Steven Lei Updated description
" 02/03/23 Steven Lei Added equations for adder/subtractor and flags
" 02/03/23 Steven Lei Added comments explaining code

" Pins

" Inputs

Subtract pin 37; "input Add/Subtract input (low for add)

" Operand A input

A3 pin 31; "input operand A, bit 3
A2 pin 30; "input operand A, bit 2
A1 pin 29; "input operand A, bit 1
A0 pin 26; "input operand A, bit 0

" Operand B input

B3 pin 22; "input operand B, bit 3
B2 pin 21; "input operand B, bit 2
B1 pin 20; "input operand B, bit 1
B0 pin 19; "input operand B, bit 0

" Sum/Difference output

Sum4	pin 13	ISTYPE 'COM';	"output	Sum/Difference, bit 4
Sum3	pin 3	ISTYPE 'COM';	"output	Sum/Difference, bit 3
Sum2	pin 2	ISTYPE 'COM';	"output	Sum/Difference, bit 2
Sum1	pin 44	ISTYPE 'COM';	"output	Sum/Difference, bit 1
Sum0	pin 43	ISTYPE 'COM';	"output	Sum/Difference, bit 0

" Flag outputs

Carry	pin 9	ISTYPE 'COM';	"output	Carry flag
Overflow	pin 8	ISTYPE 'COM';	"output	Overflow flag
Sign	pin 7	ISTYPE 'COM';	"output	Sign flag
Zero	pin 4	ISTYPE 'COM';	"output	Zero flag

" Comparison outputs

UnsignedGT	pin 15	ISTYPE 'COM';	"output	unsigned greater than (>)
UnsignedEQ	pin 41	ISTYPE 'COM';	"output	unsigned equal to (=)
UnsignedLT	pin 24	ISTYPE 'COM';	"output	unsigned less than (<)
SignedGT	pin 16	ISTYPE 'COM';	"output	signed greater than (>)
SignedEQ	pin 42	ISTYPE 'COM';	"output	signed equal to (=)
SignedLT	pin 25	ISTYPE 'COM';	"output	signed less than (<)

" Unconnected Pins

"IOA13	pin 14		input/output
"IOB0	pin 18		input/output
"IOB12	pin 35		input/output
"IOB13	pin 36		input/output
"IOGOE0	pin 40		input/output/output enable
"IOGOE1	pin 38		input/output/output enable
"ICLK0	pin 39		input/clock
"ICLK2	pin 17		input/clock

" Programming Pins (not available for use in the design)

"TCK	pin 10	pgm	programming interface TCK
"TDI	pin 1	pgm	programming interface TDI
"TDO	pin 32	pgm	programming interface TDO
"TMS	pin 23	pgm	programming interface TMS

" Power Pins

"GND	pin 5	supply	power	ground
"GND	pin 12	supply	power	ground
"GND	pin 27	supply	power	ground
"GND	pin 34	supply	power	ground
"VCC	pin 11	supply	power	Vcc
"VCC	pin 33	supply	power	Vcc
"VCCIO	pin 28	supply	power	Vcc I/O
"VCCIO	pin 6	supply	power	Vcc I/O

" Intermediate Terms

CarryOut0	node	ISTYPE 'COM';	"node	carry out of bit 0
CarryOut1	node	ISTYPE 'COM';	"node	carry out of bit 1
CarryOut2	node	ISTYPE 'COM';	"node	carry out of bit 2

EQUATIONS

" The equations for each sum bit and carry bit are generated by implementing
 " the add/ subtracter design in HW3. The B inputs must be XOR'd with subtract
 " to account for subtraction. The carry in for the 0 bit is just subtract.

```
Sum0 = (A0 $ (B0 $ Subtract)) $ Subtract;
Sum1 = (A1 $ (B1 $ Subtract)) $ CarryOut0;
Sum2 = (A2 $ (B2 $ Subtract)) $ CarryOut1;
Sum3 = (A3 $ (B3 $ Subtract)) $ CarryOut2;
```

```
CarryOut0 = (A0 & (B0 $ Subtract)) # ((A0 $ (B0 $ Subtract)) & Subtract);
CarryOut1 = (A1 & (B1 $ Subtract)) # ((A1 $ (B1 $ Subtract)) & CarryOut0);
CarryOut2 = (A2 & (B2 $ Subtract)) # ((A2 $ (B2 $ Subtract)) & CarryOut1);
```

" Note that the last sum bit is the carryout of the previous sum bit.

```
Sum4 = (A3 & (B3 $ Subtract)) # ((A3 $ (B3 $ Subtract)) & CarryOut2);
```

" FLAGS

" The flags describe the output of the adder/subtractor.

" Zero = if the sum/difference is 0

" Carry = carryout of the last bit (sum4)

" Sign = sign bit of a signed number

" Overflow = if the sum/difference is beyond the bounds (0,15) or (-8,7)

```
Zero = (!Sum0 & !Sum1 & !Sum2 & !Sum3);
```

" The carry is the last carryout bit (Sum4). But since the signal
 " needs to be active high carry/borrow it needs to be XOR'd with
 " subtract for correction.

```
Carry = Sum4 $ Subtract;
```

```
Sign = Sum3;
```

```
" The overflow equation can be solved by treating all  
" cases as addition (since subtraction is the same as  
" adding the negative). Overflow occurs in addition  
" either when pos + pos = neg or neg + neg = pos.
```

```
Overflow = (Sum4 & !CarryOut2) # (!Sum4 & CarryOut2);
```

```
" Unsigned comparisons using flags only (assuming subtraction)
```

```
UnsignedEQ = Zero;
```

```
" For UnsignedGT, there should be no carry (overflow applies only for signed)  
" if A > B (all solutions are between A-B=0 and A-B = A)
```

```
UnsignedGT = (!Carry & !Zero);
```

```
" less than is just not greater than or equal  
UnsignedLT = !(UnsignedGT # UnsignedEQ);
```

```
" Signed comparisons using flags only (assuming subtraction)
```

```
SignedEQ = Zero;
```



```
" For SignedGT, there are three comparison cases to consider:  
" for positive A, positive B -> no overflow, no carry, no sign  
" for positive A, negative B, -> could be overflow, always carry, sign depends on  
overflow  
" for negative A, negative B, -> no overflow, no carry, no sign
```

```
SignedGT = !Zero & ((!Carry & !Sign & !Overflow) # (Carry & !(Sign $ Overflow)));
```

```
" less than is just not greater than or equal  
SignedLT = !(SignedGT # SignedEQ);
```

```
END addsub
```

4bit Adder:

  

Add/Sub Equation

$$\begin{aligned} S_0 &= (B_0 \oplus Sub) \oplus A_0 \oplus C_{out0} & C_{out0} &= A_0 (B_0 \oplus Sub) + (A_0 \oplus B_0) Sub \\ S_1 &= ((B_1 \oplus Sub) \oplus A_1) \oplus C_{out1} & C_{out1} &= A_1 (B_1 \oplus Sub) + (A_1 \oplus B_1) C_{out0} \\ S_2 &= ((B_2 \oplus Sub) \oplus A_2) \oplus C_{out2} & C_{out2} &= A_2 (B_2 \oplus Sub) + (A_2 \oplus B_2) C_{out1} \\ S_3 &= ((B_3 \oplus Sub) \oplus A_3) \oplus C_{out3} \\ S_4 &= (A_3 (B_3 \oplus Sub) + A_3 \oplus (B_3 \oplus Sub)) C_{out2} & C_{out3} &= (A_3 \oplus B_3) Sub \end{aligned}$$

$$Zero = \overline{S_3} \overline{S_2} \overline{S_1} \overline{S_0}$$

Overflow: Only for signed

$$Sign = S_3$$

$$Carry = S_4$$

Subtraction can be treated as addition:

Case 1:		Case 2:
+ Positive	$\begin{array}{r} 0111 \\ + 0111 \\ \hline 0111 \end{array}$	+ Negative
+ Positive	$\begin{array}{r} 00111 \\ + 0111 \\ \hline 01110 \end{array}$	+ Negative
Negative	$\begin{array}{r} 01110 \\ - 0111 \\ \hline 01110 \end{array}$	Positive

$$C_{out2} S_4 + C_{out2} S_4 = C_{out2} \oplus S_4$$

2's complement

$$0 \rightarrow \text{min} \rightarrow \text{max} \rightarrow -8 \rightarrow \text{min} \rightarrow -1$$

Unsigned Comparisons

$$1010 = 1010 \rightarrow Zero = \text{UnSign } E_4$$

$$\begin{aligned} 1010 &> 1001 & C: 0 \\ 10 &- 9 & S: X \text{ - shouldn't matter} \\ \text{cannot overflow} & & Z: 0 \\ 1010 &> 0001 & C: 0 \\ & & S: X \\ & & Z: 0 \end{aligned}$$

$$\text{UnSign LT} = (\text{UnSign } E_4 + \text{UnSign } S_4)$$

$$\overline{C} \overline{Z} = \text{UnSigned GT}$$

Sign Comparisons

$$1001 - 1001 = Zero = \text{Sign } E_4$$

$$+A > +B$$

$$\begin{aligned} C: 0 \\ S: 0 \\ Z: 0 \\ O: 0 \end{aligned}$$

$$+A > -B$$

$$\begin{aligned} C: A \text{ (ways)} \\ S: \text{could be negative or not depending on overflow} \\ Z: 0 \\ O: \text{could overflow or not} \end{aligned}$$

Since $|A| < |B|$, then $-A < -B$

$$-A > -B$$

$$\begin{aligned} C: 0 \\ S: 0 \\ Z: 0 \\ O: 0 \end{aligned}$$

$$\begin{aligned} A > B & \quad A < B \\ -5: 1011 & \quad 1011 - 5 \\ -6: 1010 & \quad 0100 - (-4) \\ \text{Carry} & \quad \text{Carry} \\ \text{out} & \quad \text{out} \\ \text{out} & \quad \text{out} \end{aligned}$$

Carry for subtraction: Bout

$$Z (\overline{C} \overline{S} + C (0 \oplus S)) = \text{Signed GT}$$

$$\begin{aligned} & \begin{array}{ccc} 1 & 1 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{array} = \text{XOR} \end{aligned}$$

Similar to...

Carry
for subtraction: Borrow

0 0 1

$$\text{Signed LT} = \overline{(\text{Signed GT}) + \text{Zero}}$$